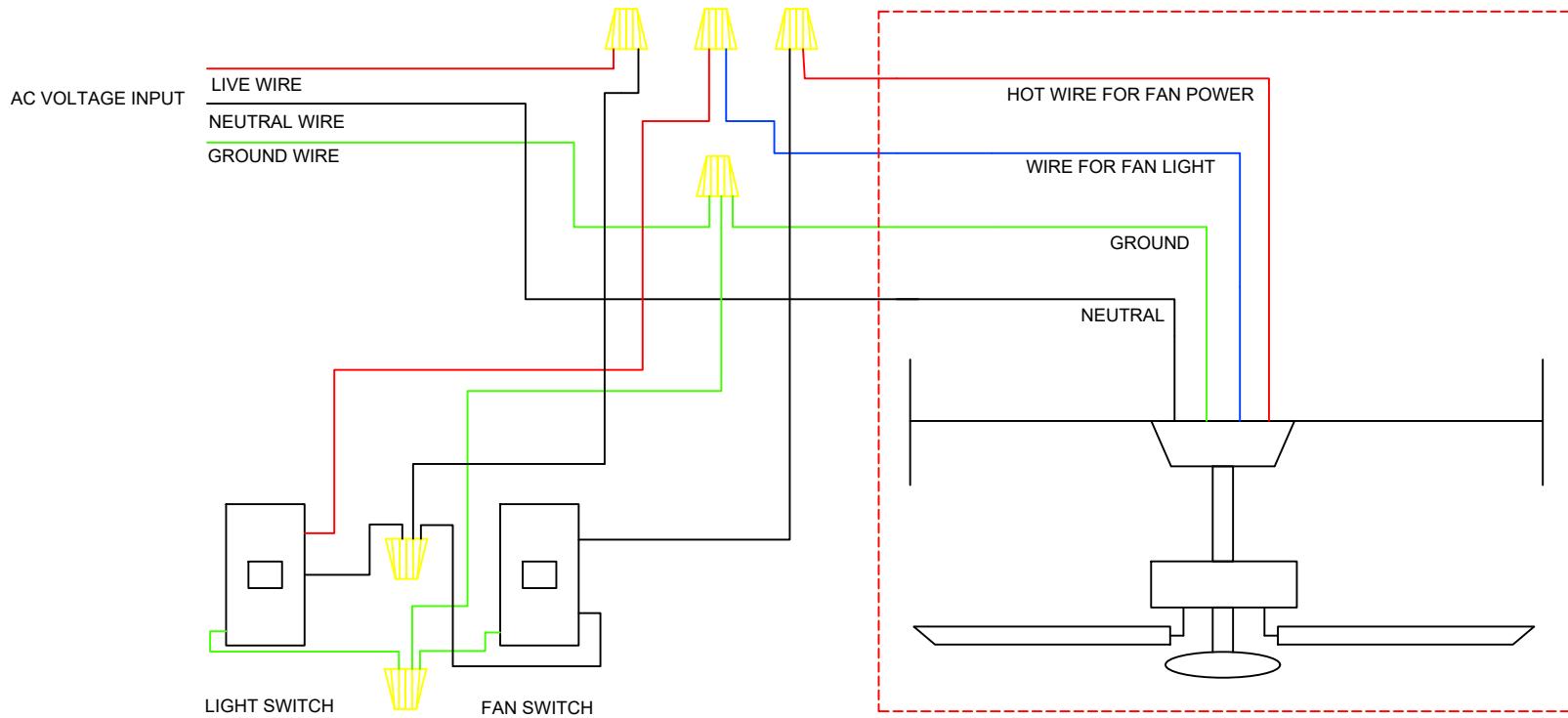


4 WIRE CEILING FAN WIRING DIAGRAM



4 WIRE CEILING WIRING DIAGRAM BASIC GUIDE:

What "4-Wire Ceiling Fan" Means?

A ceiling fan with 4 wires allows separate control of:

- Fan motor
- Light

So you can use two wall switches (one for fan, one for light).

If You Have Only ONE Wall Switch

Connect fan Hot + fan blue together
Connect them to house red
Fan and light turn on together

Important Safety Notes

- Turn power OFF at the breaker
- Use wire nuts properly
- Secure fan to a fan-rated box

Common Problems

- Fan works but light doesn't → red wire not connected
- Light works but fan doesn't → black wire not connected
- Nothing works → neutral (white) issue